

UCSC Extension – Digital Design with FPGA

Jae-Yang Park (jaeyangp@gmail.com)

Problem 2.6.1

1. Show that lutmask 8000 implements 4-inputs AND gate

a	b	c	d	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

$$F = a b c d$$

$$\text{LUTMASK} = 8000$$

2. Implement a 4 inputs XOR gate using a LUT4

a	b	c	d	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$F = a'b'c'd + a'b'cd' + a'bc'd' + a'bc'd + ab'c'd' + ab'cd + abc'd + abcd'$$

$$\text{LUTMASK} = 6996$$

3. Implement the function below using a LUT4

a	b	c	d	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$$F = abcd + a'b'c'd' + ad' + a'bc' + b'd + a'bc' + abc'd + bcd + a'cd'$$


$$= \text{TAUTOLOGY}$$

LUTMASK = FFFF

Problem 2.6.2

1. Implement all the 16 possible two-input functions using the above block
Complete the table as follows:


		a0	a1	sa	b0	b1	sb	s0	s1
1	XOR (a, b)	0	1	b	1	0	b	a	0
2	AND (a, b)	0	0	b	0	1	b	a	0
3	OR (a, b)	0	1	b	1	1	b	a	0
4	NAND (a, b)	1	1	b	1	0	b	a	0
5	NOR (a, b)	1	0	b	0	0	b	a	0
6	XNOR (a, b)	1	0	b	0	1	b	a	0
7	A < B	0	1	b	0	0	b	a	0
8	A > B	0	0	b	1	0	b	a	0
9	A LE B	1	1	b	0	1	b	a	0
10	A GE B	1	0	b	1	1	b	a	0
11	BUFFER (A)	0	0	b	1	1	b	a	0
12	BUFFER (B)	0	1	b	1	1	b	a	0
13	NOT (A)	1	1	b	0	0	b	a	0
14	NOT (B)	1	0	b	1	0	b	a	0
15	CONTRIDITION	0	0	b	0	0	b	a	0
16	TAUTOLOGY	1	1	b	1	1	b	a	0

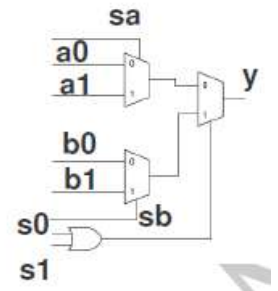


2. Implement $f = ab + b'c + d$ using the above block





a	b	c	d	ab	b'c	ab+b'c+d
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	0	1	1	0	1	1
0	1	0	0	0	0	0
0	1	0	1	0	0	1
0	1	1	0	0	0	0
0	1	1	1	0	0	1
1	0	0	0	0	0	0
1	0	0	1	0	0	1
1	0	1	0	0	1	1
1	0	1	1	0	1	1
1	1	0	0	1	0	1
1	1	0	1	1	0	1
1	1	1	0	1	0	1
1	1	1	1	1	0	1

		a0	a1	sa	b0	b1	sb	s0	s1
1	AND (a, b)	0	0	b	0	1	b	a	0
3	OR (a, b)	0	1	b	1	1	b	a	0

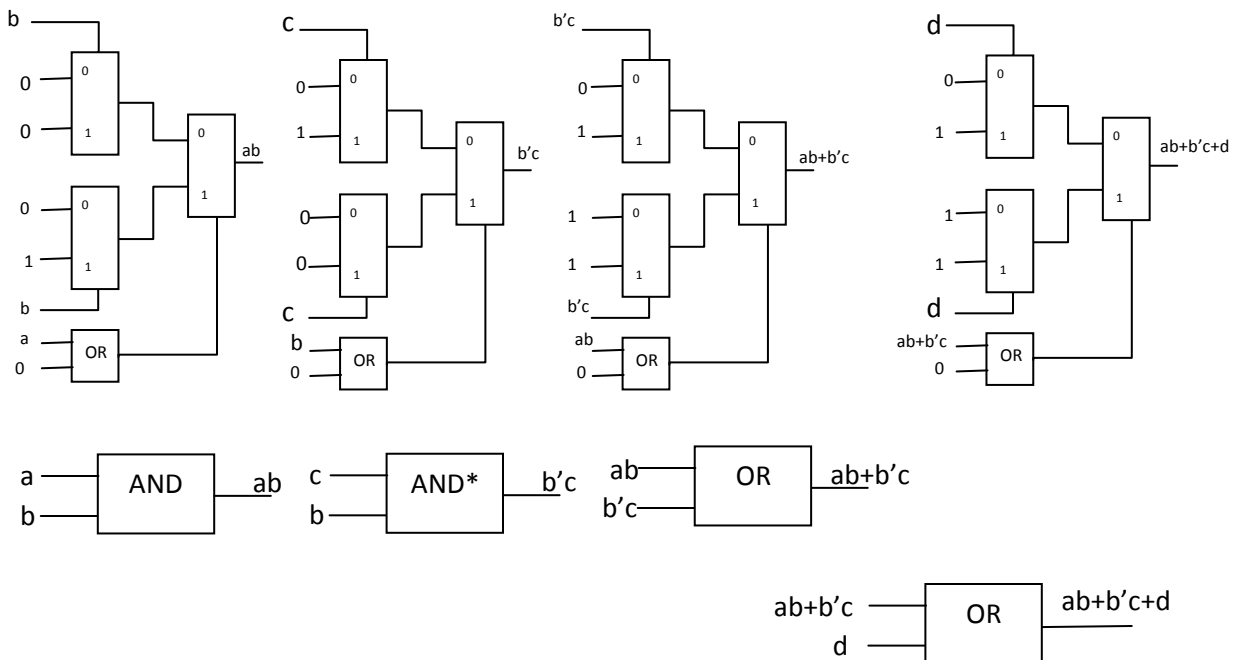

 


Problem 3.7.1

 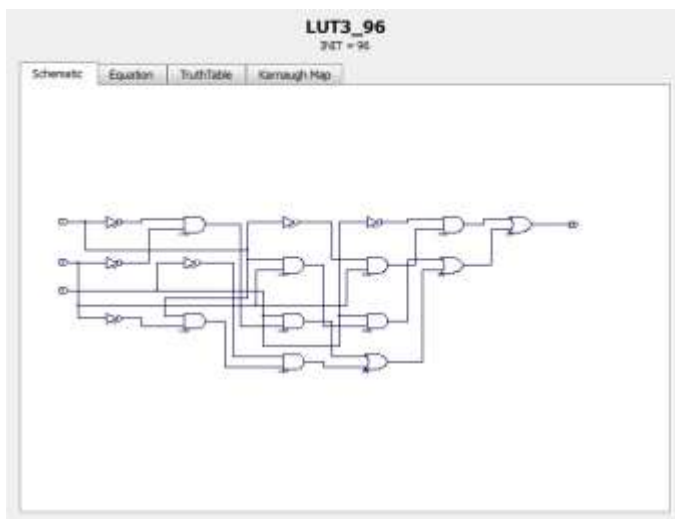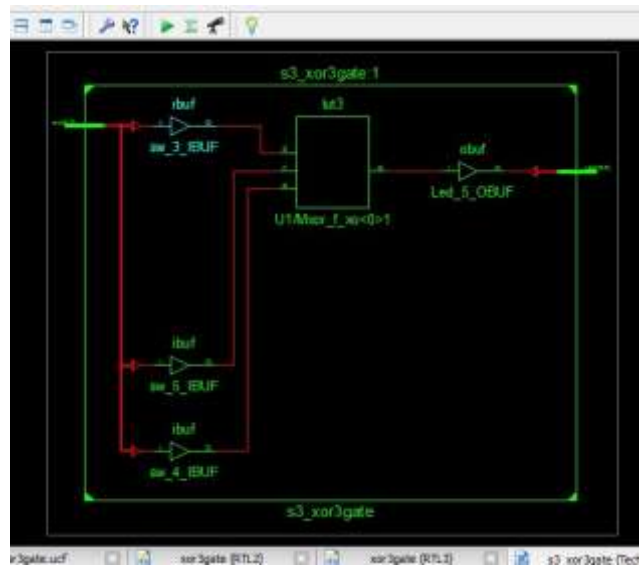 

LUT3_96
DIT = 96

I2	I1	I0	Q
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

```

1  `timescale 1ns / 1ps
2  //////////////////////////////////////////////////
3  // Company: UCSC Extension - Digital Design with FPGA
4  // Engineer: Jae-Yang Park
5  //
6  // Create Date:    19:12:43 01/27/2014
7  // Design Name:
8  // Module Name:    xor3gate
9  // Project Name:
10 // Target Devices:
11 // Tool versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 //////////////////////////////////////////////////
21 module xor3gate(a, b, c, f);
22     input a, b, c;
23     output f;
24
25     assign f = a ^ b ^ c;
26 endmodule
27
28 module s3_xor3gate(sw, Led);
29     input    [5:3] sw;
30     output   [5:5] Led;
31
32     xor3gate U1 (.a(sw[5]), .b(sw[4]), .c(sw[3]), .f(Led[5]));
33 endmodule

```

```

1  # FILE:xor3gate.ucf
2
3  # Pin assignment for SWITCHES
4  NET "sw<5>" LOC = "F3";
5  NET "sw<4>" LOC = "G3";
6  NET "sw<3>" LOC = "B4";
7
8
9  # Pin assignment for LEDs
10 NET "Led<5>" LOC = "N4" ;
11

```

SW5	SW4	SW3	
OFF	OFF	OFF	
OFF	OFF	ON	
OFF	ON	OFF	
OFF	ON	ON	

ON	OFF	OFF	
----	-----	-----	--

LUT4_FEE8 INIT = FEE8				
Schematic	Equation	TruthTable	Karnaugh Map	
I3	I2	I1	I0	O
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

LUT4_FEE8 INIT = FEE8				
Schematic	Equation	TruthTable	Karnaugh Map	

```

1  `timescale 1ns / 1ps
2  //////////////////////////////////////
3  // Company: UCSC Extension - Digital Design with FPGA
4  // Engineer: Jae-Yang Park
5  //
6  // Create Date:    19:09:53 01/28/2014
7  // Design Name:
8  // Module Name:    maj4
9  // Project Name:
10 // Target Devices:
11 // Tool versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 //////////////////////////////////////
21 module maj4(a, b, c, d, f);
22     input a, b, c, d;
23     output f;
24
25     assign f = (a & b) | (a & c) | (a & d) | (b & c) | (b & d) | (c & d);
26 endmodule
27
28 module s3_maj4(sw, Led);
29     input [6:3] sw;
30     output [3:3] Led;
31
32     maj4 U1 (.a(sw[6]), .b(sw[5]), .c(sw[4]), .d(sw[3]), .f(Led[3]));
33
34 endmodule
35











```




```

1  # FILE:maj4.ucf
2
3  # Pin assignment for SWITCHES
4  NET "sw<6>" LOC = "E2";
5  NET "sw<5>" LOC = "F3";
6  NET "sw<4>" LOC = "G3";
7  NET "sw<3>" LOC = "B4";
8
9  # Pin assignment for LEDs
10 NET "Led<3>" LOC = "P6" ;
11

```

SW6	SW5	SW4	SW3	
OFF	OFF	OFF	OFF	
OFF	OFF	OFF	ON	

OFF	OFF	ON	OFF		
OFF	OFF	ON	ON		
OFF	ON	OFF	OFF		
OFF	ON	OFF	ON		
OFF	ON	ON	OFF		
OFF	ON	ON	ON		
ON	OFF	OFF	OFF		
ON	OFF	OFF	ON		
ON	OFF	ON	OFF		
ON	OFF	ON	ON		

ON	ON	OFF	OFF		
ON	ON	OFF	ON		
ON	ON	ON	OFF		
ON	ON	ON	ON	