

## UCSC Extension - Digital Design using FPGA

### HW #4

Jae-Yang Park ([jaeyangp@gmail.com](mailto:jaeyangp@gmail.com))

### Problem 3.7.6 One minute counter

#### Code

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company: UCSC Extension - Digital Design using FPGA
// Engineer: Jae-Yang Park
//
// Create Date: 18:45:09 02/09/2014
// Design Name: Problem 3.7.6
// Module Name: oneminute
/////////////////////////////////////////////////////////////////
module counter(clk, arst, en, q);
    parameter N = 7;

    input clk, arst, en;
    output [N-1:0] q;
    reg [N-1:0] q;

    always @(posedge clk or posedge arst)
        if (arst == 1'b1)
            q <= 0;
        else if (en)
            q <= q + 1;
endmodule

module mod_counter(clk, arst, q, done);
    parameter N = 7;
    parameter MAX = 127;

    input clk, arst;
    output [N-1:0] q;
    output done;
    reg [N-1:0] q;
    reg done;

    always @(posedge clk or posedge arst) begin
        if (arst == 1'b1) begin
            q <= 0;
            done <= 0;
        end
        else if (q == MAX) begin
            q <= 0;
            done <= 1;
        end
        else begin
            q <= q + 1;
        end
    end
endmodule
```

```

        done <= 0;
    end
end
endmodule

module oneminute(CLK1, arst, seg, an, Led);
    parameter C = 33; // counter,
    parameter N = 7; // seven segment
    parameter W = 4; // size of binary number, # of Led
    parameter CRYSTAL = 50; // 50MHz
    parameter NUM_SEC = 60;
    parameter [C-1:0] STOPAT = (CRYSTAL * 1_000_000 * NUM_SEC) - 1;

    input CLK1, arst;
    output [0:N-1] seg;
    output [3:0] an;
    output [W-1:0] Led;
    wire [C-1:0] clock;
    wire [W-1:0] zero_to_f_counter;
    wire one_min_clock;

    assign an = 4'b0000;

    mod_counter #(C, STOPAT) U1 (.clk(CLK1), .arst(arst), .q(clock), .done(one_min_clock));
    counter #(W) S (.clk(CLK1), .arst(arst), .en(one_min_clock), .q(zero_to_f_counter));
    hex2_7seg_lut D (zero_to_f_counter, seg);

    assign Led = zero_to_f_counter;
endmodule

```

In order to make one minute counter, follow parameters in the module oneminute are changed:

**parameter C = 33**

Counting value for one minute is  $50 * 10^6 * 60 - 1$  is 2999999999, and 33 bits counter is needed.

**parameter NUM\_SEC = 60**

One minute is 60 seconds





**parameter [C-1:0] STOPAT = (CRYSTAL \* 1\_000\_000 \* NUM\_SEC) - 1**

For 60 sec counter, this STOPAT value is 2999999999, and it needs 33 bits.

Default integer value needs 32 bits. If the width is not mentioned, Xilinx tools can't place and route this value, and display warning messages:

**Command Line:** bitgen -intstyle ise -f oneminute.ut oneminute.ncd

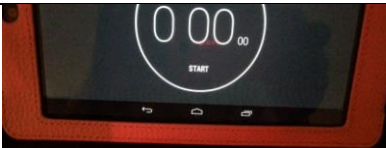**WARNING:PhysDesignRules:367 - The signal <CLK1\_IBUF> is incomplete. The signal does not drive any load pins in the design.**

Start: 0 Sec	 
After 1 minute	 

### Problem 3.7.7 Display all possible patterns on the seven segment

#### Code

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company: UCSC Extension - Digital Design using FPGA
// Engineer: Jae-Yang Park
//
// Create Date: 19:59:51 02/16/2014
// Design Name: Problem 3.7.7
// Module Name: disp_all_pattern
/////////////////////////////////////////////////////////////////

module mod_counter(clk, arst, q, done);
    parameter N = 7;
    parameter MAX = 127;

    input clk, arst;
    output [N-1:0] q;
    output done;
    reg [N-1:0] q;
    reg done;

    always @(posedge clk or posedge arst) begin
        if (arst == 1'b1) begin
            q <= 0;
            done <= 0;
        end
        else if (q == MAX) begin
            q <= 0;
            done <= 1;
        end
        else begin
            q <= q + 1;
            done <= 0;
        end
    end
end
endmodule

module disp_all_pattern(CLK1, arst, seg, an);
    parameter N = 7; // seven segment
    parameter C = 27; // counter,
    parameter CRYSTAL = 50; // 50MHz
    parameter NUM_SEC = 1;
    parameter STOPAT = (CRYSTAL * 1_000_000 * NUM_SEC) - 1;

    input CLK1, arst;
    output [0:N-1] seg;
    output [3:0] an;
    reg [0:N-1] seg;
    reg [3:0] an;
```

```

mod_counter #(C, STOPAT) U1 (.clk(CLK1), .arst(arst), .done(one_sec_clock));



always @ (posedge one_sec_clock or posedge arst) begin
    if (arst == 1'b1) begin
        seg <= 7'b111_1111;
        an <= 4'b1111;
    end
    else begin
        seg <= seg - 1;
        an <= 4'b0000;
    end
end

endmodule

```

**The number of all possible patterns** =  $2^7 - 1 = 127$  patterns (because when 7'b0000000, all LEDs on the segment are OFF)

  **Total time to display all possible patterns** = **127 seconds** (every one second different pattern is displayed)



### Problem 3.7.8 Heart beat pattern

#### Code

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company: UCSC Extension-Digital Design using FPGA
// Engineer: Jae-Yang Park
//
// Create Date: 12:21:12 02/17/2014
// Design Name: Problem 3.7.8
// Module Name: heart_beat
// Project Name:
/////////////////////////////////////////////////////////////////

`define USQUARE 7'b0011100
`define DSQUARE 7'b1100010

module mod_counter(clk, arst, q, done);
    parameter N = 7;
    parameter MAX = 127;

    input clk, arst;
    output [N-1:0] q;
    output done;
    reg [N-1:0] q;
    reg done;

    always @(posedge clk or posedge arst) begin
        if (arst == 1'b1) begin
            q <= 0;
            done <= 0;
        end
        else if (q == MAX) begin
            q <= 0;
            done <= 1;
        end
        else begin
            q <= q + 1;
            done <= 0;
        end
    end
end
endmodule

module heart_beat(CLK1, arst, seg, an);
    parameter N = 7; // seven segment
    parameter C = 27; // counter,
    parameter CRYSTAL = 50; // 50MHz
    parameter NUM_SEC = 1;
    parameter STOPAT = (CRYSTAL * 1_000_000 * NUM_SEC) - 1;

    input CLK1, arst;
    output [0:N-1] seg;
```

```

output [3:0] an;
reg [0:N-1] seg;
reg [3:0] an, up_an, down_an;
reg [2:0] shift_count;
reg up_down;    // 0: up, 1: down square

// one second counter
mod_counter #(C, STOPAT) U1 (.clk(CLK1), .arst(arst), .done(one_sec_clock));

always @ (posedge one_sec_clock or posedge arst) begin
    if (arst == 1'b1) begin
        seg <= `USQUARE;
        an <= 4'b1111;
        up_an <= 4'b0111;
        down_an <= 4'b1110;
        shift_count <= 3'b000;
        up_down <= 1'b0;    // 0: upper square, 1: down
    end
    else begin
        if (up_down == 1'b0) begin
            seg <= `USQUARE;
            an <= up_an;
            up_an <= {up_an[0], up_an[3:1]}; // rotate 1 bit right

            if (shift_count == 3'b011) begin
                up_down <= 1'b1;
                up_an <= 4'b0111;
            end
        end
        else if (up_down == 1'b1) begin
            seg <= `DSQUARE;
            an <= down_an;
            down_an <= {down_an[2:0], down_an[3]}; // rotate 1 bit left

            if (shift_count == 3'b111) begin
                up_down <= 1'b0;
                down_an <= 4'b1110;
            end
        end
        shift_count <= shift_count + 1;
    end
end
endmodule

```

